

# LC Tank with Resistance

Vinod Kumar Metla

*Roll No. : 130010048*

October 23, 2016

### **Abstract**

The problem is to simulate the behaviour of a LC tank with a resistance applied across a voltage in series with given initial conditions of the charge in the capacitor and current in the inductor.

- Public git repo with open source code is available on [https://github.com/vinodm24/sdes\\_project\\_1](https://github.com/vinodm24/sdes_project_1)
- Ipython 2.3.0 is used to run the IPython notebook. So the version 2.3.0 or higher is preferable to run the notebook.
- numpy version 1.8.2 is used. So numpy version 1.8.2 or higher is preferred to run the code.
- matplotlib version 1.4.2 is used. So matplotlib version 1.4.2 or higher is preferred to run the code.

## Governing Equation for the problem

The governing equation for this electrical problem is

$$\frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{Q}{LC} = \frac{V}{C} \quad (1)$$

where  $Q$  is the charge in the capacitor varying with time,  $R$  is the resistance in the circuit,  $L$  is inductance of the inductor,  $C$  is the capacitance of the capacitor and  $V$  is the voltage of the source voltage under the initial conditions of  $Q(0^+) = Q_0$  the initial charge in the capacitor and  $\frac{dQ}{dt}(0^+) = i_0$ , where initial inductor current is  $i_0$ .

Solving this analytically for two cases of  $\Delta = 0$  and  $\Delta \neq 0$  where  $\Delta = \frac{R^2}{L^2} - \frac{4}{LC}$

$\Delta = 0$  :

The solution when  $\Delta = 0$  under the given initial conditions is:

$$Q(t) = CV + e^{\frac{-2Lt}{R}}(C_1t + C_2) \quad (2)$$

where  $C_1 = i_0 + \frac{R}{2L}(Q_0 - CV)$ ,  $C_2 = (Q_0 - CV)$

$\Delta \neq 0$  :

The solution when  $\Delta \neq 0$  under the given initial conditions is:

$$Q(t) = CV + A_1e^{s_1t} + A_2e^{s_2t} \quad (3)$$

where  $s_1 = \frac{-R}{2L} + \frac{\sqrt{\Delta}}{2}$ ,  $s_2 = \frac{-R}{2L} - \frac{\sqrt{\Delta}}{2}$   
 $A_1 = \frac{i_0 - (Q_0 - CV)s_2}{s_1 - s_2}$ ,  $A_2 = \frac{i_0 - (Q_0 - CV)s_1}{s_2 - s_1}$

The results were plotted showing the voltage across all the elements of the circuit varying with time for three cases of damping.

### Under Damped case

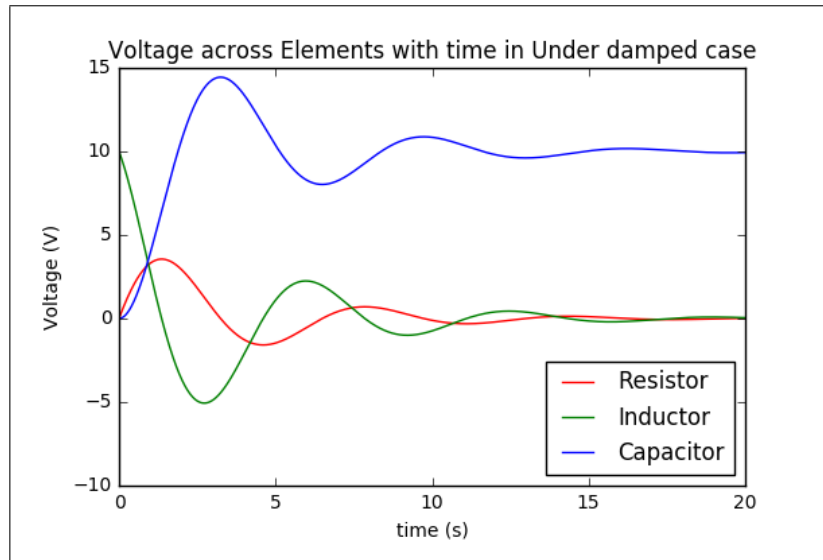


Figure 1: *Voltage vs time* <sup>1</sup>.

### Critically Damped case

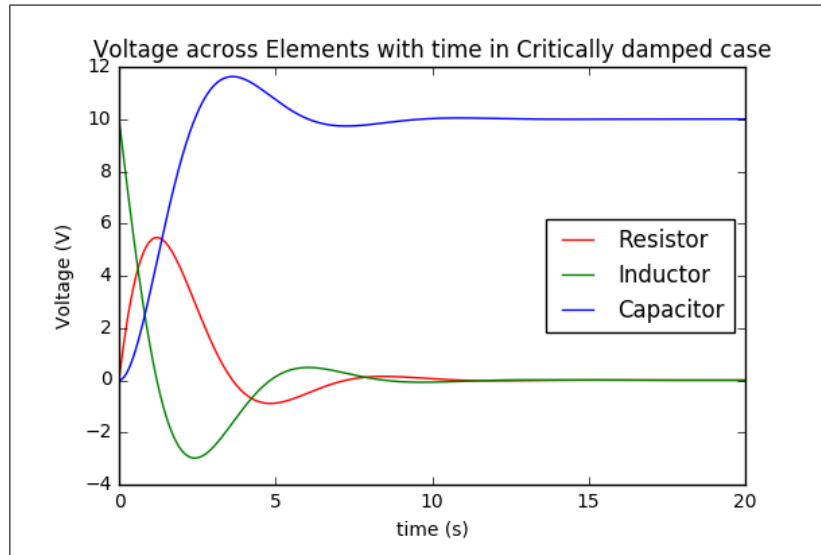


Figure 2: *Voltage vs time*<sup>2</sup>.

### Over Damped case

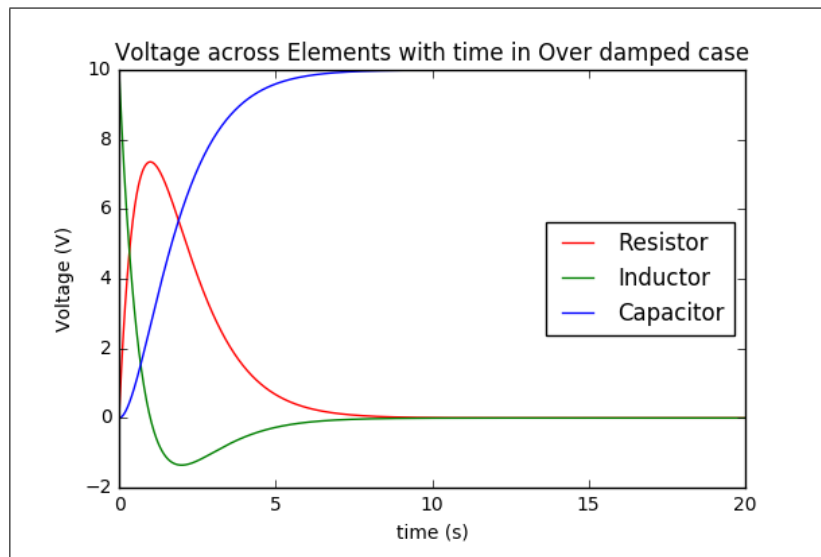


Figure 3: *Voltage vs time*<sup>3</sup>.